



Notes:

A PLLXO is the simplest line level XO that can be used with these. The 1st order version preserves phase & with the drivers within 1/4 wavelength at the XO point should maintain phase coherence. Actual values (for the HP) are dependent on the input impedance of the amplifier. It will also perform best with a pre-amp with low output impedance